

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY, TUMKUR.

(A Constituent College of Sri Siddhartha Academy of Higher Education, Agalakote, Tumkur.)

B.E., SEMESTER END EXAMINATION (SUMMER) – SEPT/OCT 2021

ES-EEI102 / ES-EE101 : BASIC ELECTRICAL ENGINEERING

TIME: 3.00 Hrs

SEMESTER : I

MAX MARKS: 100

NOTE: Answer any five full questions by choosing at least one full question from Unit-1 to Unit-4 and 5th question can be from Unit-1 to Unit-5.

UNIT-1

- | | M | CO | BL |
|---|----|----|-------|
| 1.a) Sketch the sinusoidal alternating current wave form and define the following terms. | 06 | 1 | 1,2 |
| i. Instantaneous value | | | |
| ii. Amplitude | | | |
| iii. Cycle | | | |
| iv. Time period | | | |
| v. Frequency | | | |
| b) Examine whether the current in a pure capacitor leads the applied voltage by 90°. | 06 | 1 | 2,3 |
| c) Given $V=200\sin 377t$ volts and $I = 8\sin(377t + 30^\circ)$ for an A.C circuit. Evaluate | 08 | 3 | 3,4,7 |
| i. Power factor | | | |
| ii. Real power | | | |
| iii. Apparent power | | | |
| iv. Reactive power. | | | |

OR

- | | | | |
|---|----|---|-----|
| 2.a) Examine whether the current in a pure inductor lags the applied voltage by 90°. | 08 | 1 | 3 |
| b) Define | 05 | 1 | 1,2 |
| i. Apparent power | | | |
| ii. True power | | | |
| iii. Reactive power | | | |
| iv. Form factor | | | |
| v. Peak factor | | | |
| c) A voltage of 200Volts is applied to a series circuit consisting of resistor, inductor and capacitor. The respective voltages across the components are 170V, 150 & 100V and the current is 4A. Evaluate i. power factor ii. resistance iii. impedance. | 07 | 1 | 1,2 |

UNIT-2

- | | | | |
|---|----|---|-----|
| 3.a) Develop the relation between line and phase voltages in a three phase balanced star connected system. | 06 | 2 | 2,3 |
| b) A balanced star connected load of $(8+j6)\Omega$ per phase are connected to a three phase 400V supply. Evaluate the line current, power factor, power, reactive voltampere and total voltampere. | 06 | 2 | 2,3 |
| c) With the help of circuit diagram, explain two way and three way control of lamp. | 08 | 2 | 1,2 |

OR

- | | | | |
|---|----|---|-----|
| 4.a) Examine whether in a three phase balanced circuit, two wattmeters are sufficient to measure three phase power. | 07 | 2 | 1,2 |
| b) Two Watt meters are connected to measure power in a 3-phase unit reads 5KW and 2KW, the later reading being obtained after reversing current coil connection. Calculate power factor of load and the total power consumed. | 06 | 2 | 1,2 |
| c) With the help of neat sketch, explain plate earthing. | 07 | 2 | 1,2 |

UNIT-3

- 5.a) Define and develop an expression for co-efficient of coupling.
 b) Explain Fleming's left hand and right hand rule.
 c) Explain the principle of operation of transformer.

08	3	2,3
08	3	1,2
04	3	1,2

OR

- 6.a) Describe the construction of a single phase transformer.
 b) Develop the emf equation of a single phase transformer.
 c) A 250KVA, 11000/415 V, 50Hz single phase transformer has 80 turns on the secondary. Evaluate i. rated primary and secondary currents
 ii. number of primary turns
 iii. maximum value of flux.

07	3	1,2
07	3	1,2
06	3	2,3

UNIT-4

- 7.a) With a neat sketch, explain the construction of a D.C machine.
 b) With usual notation develop the e.m.f equation of a D C generator.
 c) An 8 pole lqp connected armature has 40 slots with 12 conductors per slot, generates a voltage of 500V. Predict the speed at which it is running if the flux per pole is 50m web.

07	4	1,2
07	4	1,2
06	4	2,3

OR

- 8.a) Explain the working principle of D C motor.
 b) Develop an expression for armature torque of a D C motor.
 c) A 200 volts series motor is taking a current of 40 amperes. Resistance of armature is 0.5Ω and resistance of series field is 0.25Ω . Evaluate back emf.

07	4	1,2
07	4	2,3
06	4	2,3

UNIT-5

- 9.a) With a neat sketch, discuss the construction and working of a 3-phase induction motor.
 b) With neat sketches, explain the concept of rotating magnetic field.
 c) A 6 pole induction motor is supplied by 10 pole alternator, which is driven at 600rpm, If the motor is running at 970 rpm, Evaluate,
 i. The percentage slip
 ii. Frequency of rotor current at full load.

08	5	1,2
06	5	1,2
06	5	2,3

OR

- 10.a) Describe the construction of an alternator.
 b) Develop the e.m.f equation of an alternator by introducing all the factors.
 c) A 4 pole, 1500 rpm star connected alternator has 9 slots per pole and 8 conductor/slot. Evaluate the flux/pole to give a terminal voltage of 3300V. Take winding factor and pitch factor as unity.

07	5	1,2
07	5	1,2
06	5	2,3
